



# Chapter4: Combinational Logic

Lecture6- Study Decoders, Function Implementation using Decoders


Engr. Arshad Nazir, Asst Prof  
Dept of Electrical Engineering  
SEECs

# Objectives

- Study design and applications of Decoders
- Function implementation using Decoder blocks
 
# Decoders

- A **decoder** is a combinational circuit that **converts** binary information from **n input** lines to a maximum of  **$2^n$**  unique **output** lines. Only one output can be active (high) at any time.
- Decoders are a class of combinational logic circuits that convert a set of input variables representing a code into a set of output variables representing a different code. The relationship between the input and output codes can be expressed in a truth table i.e 4-to-10-lines decoder circuit.
- If the n-bit coded information has **unused** combinations, the decoder has **fewer** than  $2^n$  output~



# Decoder Applications

- **Generate minterms/complement of minterms** and are used for functions implementation.
- **Memory addressing**- Decoders are widely used in the memory system of a computer where they respond to the address code generated by the central processor to activate a particular memory location.
- **Code Conversion**. Example is BCD-to-7-segment decoder.
- **DeMUX** function.
- Used in conjunction with counters to **decode (detect) counter states** and provide **timing or sequencing signals**.
- Provide **enabling inputs** when used in the design of MUXs with tri-state gates.
- Computers communicate with peripheral devices (printers, modems, scanners, keyboards, video monitors, external disk drives and other computers) by sending and/or receiving data through I/O ports. **Decoders** are used to **select I/O** as determined by the computer to receive or send data.

 


Fig. 4-18 3-to-8-Line Decoder

# Implementation of Full Adder with a Decoder

- There are three inputs and eight outputs so we need 3-to-8-line decoder
- Two **OR** gates are required for logical **sum** of the desired minterms


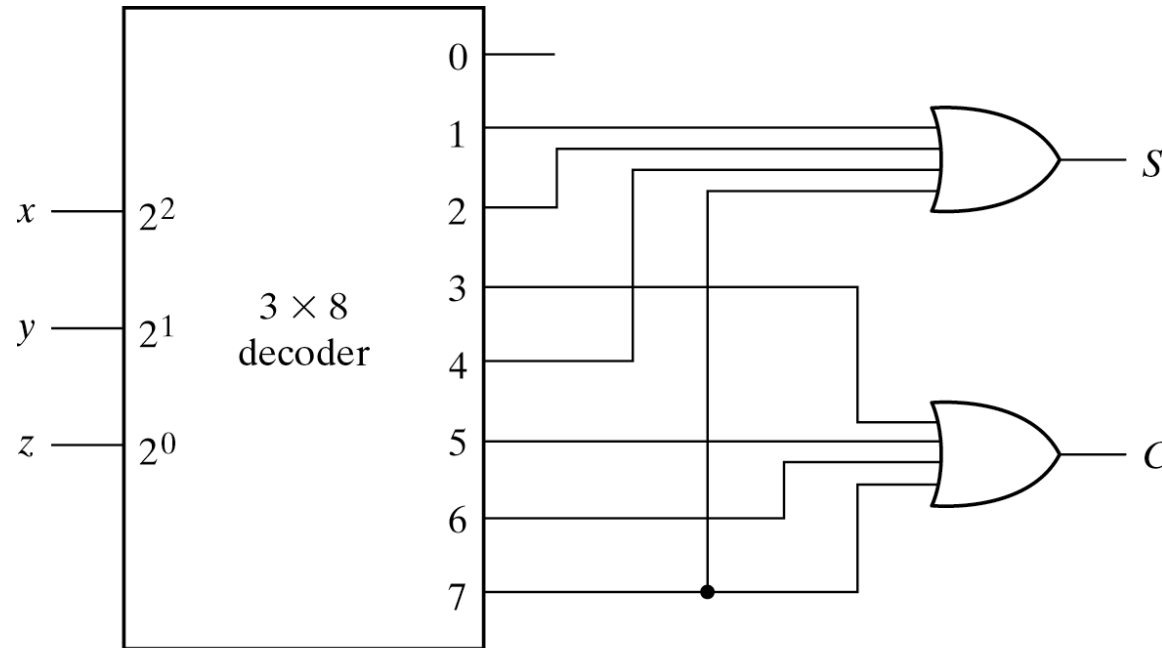


Fig. 4-21 Implementation of a Full Adder with a Decoder

 
## A very simple example

- Let's assume a very simple microprocessor with 10 address lines (1KB memory)
- Let's assume we wish to implement all its memory space and we use 128x8 memory chips
- **SOLUTION**
  - We will need 8 memory chips ( $8 \times 128 = 1024$ )
  - We will need 3 address lines to select each one of the 8 chips
  - Each chip will need 7 address lines to address its internal memory cells


 
# Decoder Example (Code Converter)


- BCD-to-seven-segment display converter is one common example of code converters, which converts one BCD digit into information suitable for driving a digit-oriented display.





 
# Demultiplexer

- A **decoder** with an enable input (Figure 4-19) can function as **demultiplexer** (1-to-4-line demultiplexer)
  - E is taken as data input line and A and B are taken as selection inputs




(a) Decoder with enable

 

(b) Demultiplexer
 
# Timing Signals Generation using Counters

- Counters may be used to generate timing signals to control the sequence of operations in a digital system.  $2^n$  timing signals can be generated using an  $n$ -bit binary counter together with an  $n$ -to- $2^n$ -line decoder



# MUX Design using Tri-State gates and Decoders

 


Fig. 4-30 Multiplexers with Three-State Gates

# 3-to-8-Line Decoder

- A 3-to-8-Line Decoder is a decoder in which three inputs are decoded into eight outputs, each representing one of the **minterms** of the **three input** variables.
- Each one of the eight AND gates generates one of the minterms.
- A particular application of this decoder is binary-to-octal conversion, however 3-to-8-line decoder can be used for decoding any 3-bit code to provide eight outputs, one for each element of the code

 


Fig. 4-18 3-to-8-Line Decoder


# 3-to-8-Line Decoder Truth Table

Inputs			Outputs							
X	Y	Z	D0	D1	D2	D3	D4	D5	D6	D7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

# Decoders with NAND gates

- Some decoders are constructed with NAND gates. Since a **NAND gate** produces the AND operation with inverted output, it becomes more economical to generate the decoder **minterms** in their **complemented** form. Decoder include one or more enable inputs to control the circuit operation
- A 2-to-4-line decoder with an enable input is shown next. (see Fig on next slide).
  - The circuit operates with complement outputs and a complement enable input.
  - The decoder is enabled when  $E$  is equal to 0 and disabled when  $E = 1$
  - The output whose value is equal to 0 represents the minterm selected by inputs  $A$  and  $B$ .
  - Only one output can be zero at any given time, all other outputs are 1
- Some decoders have two or more enable inputs that must satisfy a given logic condition

# Decoders with NAND gates

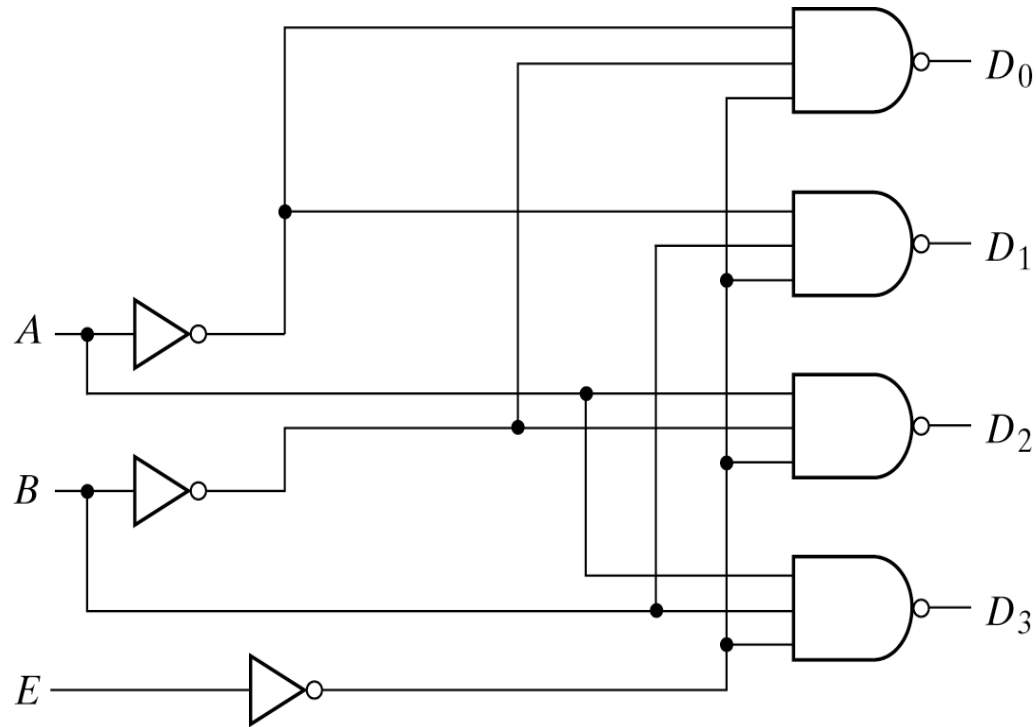

(a) Logic diagram

$E$	$A$	$B$	$D_0$	$D_1$	$D_2$	$D_3$
1	$X$	$X$	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0


(b) Truth table

Fig. 4-19 2-to-4-Line Decoder with Enable Input


 
# Demultiplexer

- A **demultiplexer** is a circuit that **receives** information from a **single** line and directs it to one of  $2^n$  possible **output** lines.
- The selection of a specific output is controlled by the bit combination of  $n$  **selection lines**.



# Constructing large Decoders

- Decoders with enable inputs can be connected together to form a **larger decoder** circuit.
  - two 3-to-8 decoder can be connected to form a 4-to-16 decoder
  - The top decoder outputs generates minterms 0000 to 0111 and the bottom decoder outputs generate minterms 1000 to 1111.


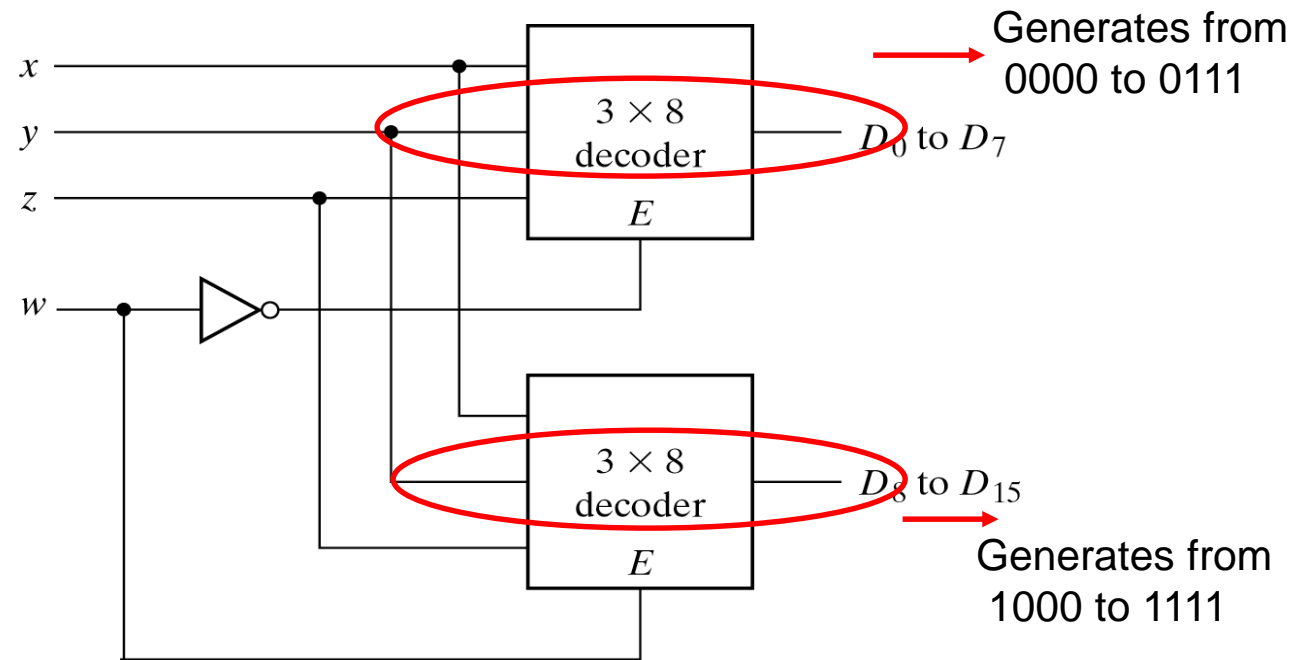


Fig. 4-20 4 × 16 Decoder Constructed with Two 3 × 8 Decoders

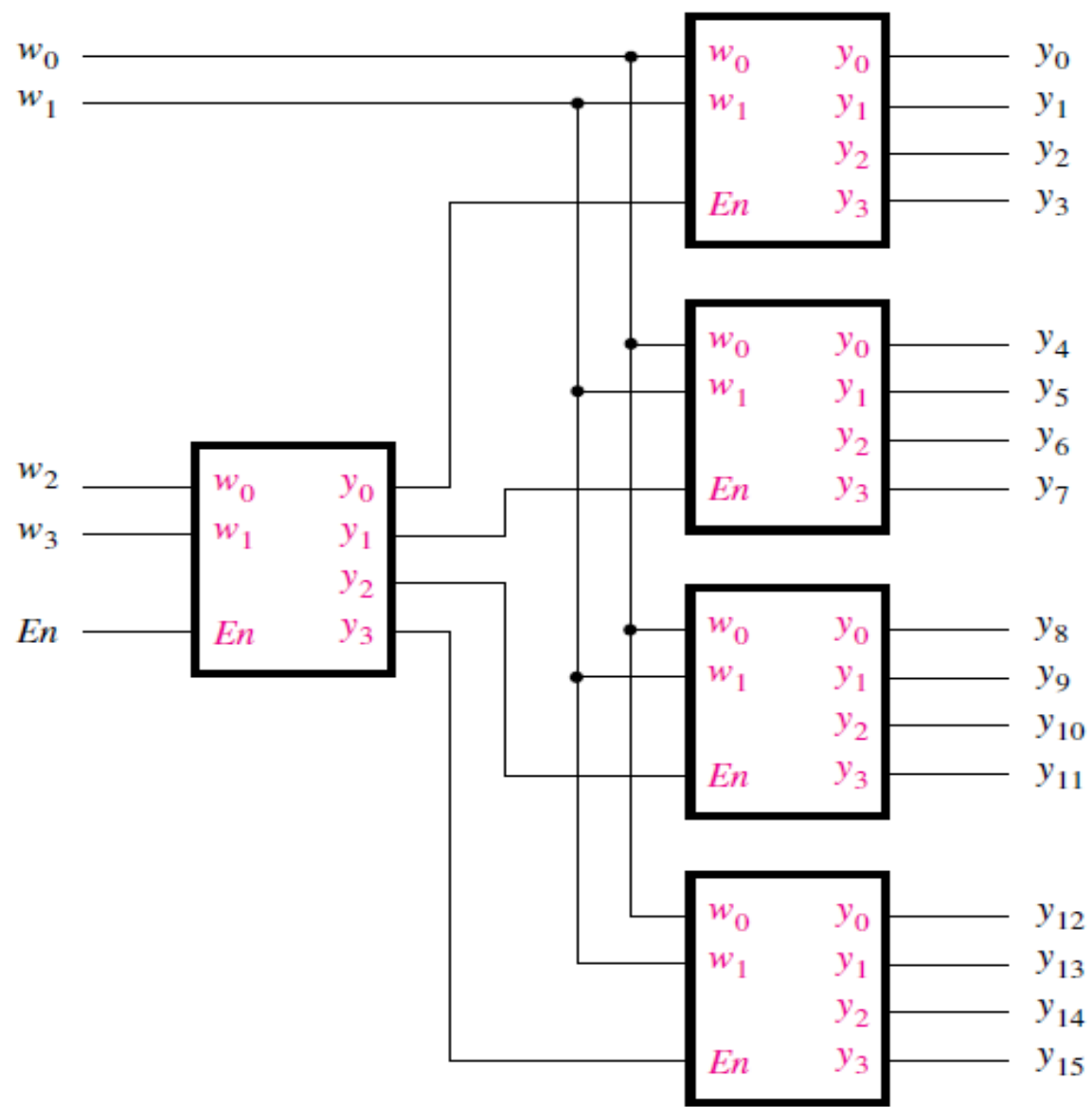

**Figure 4.16** A 4-to-16 decoder built using a decoder tree.

# Combinational Logic Implementation

- A **decoder** provides the  $2^n$  minterms of  $n$  input variables.
- Any **function** is can be expressed in **sum of minterms**.
- Use a decoder to make the minterms and an external OR gate to make the logical sum.
- In this way any combinational circuit with  $n$  inputs and  $m$  outputs can be implemented with an  $n$ -to- $2^n$  line decoder and  $m$  OR gates. Such implementation needs that the Boolean function is expressed in sum of minterms
- For example: consider a full adder.
  - $S(x,y,z) = \Sigma(1,2,4,7)$
  - $C(x,y,z) = \Sigma(3,5,6,7)$

x	y	z	c	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

# Implementation of Full Adder with a Decoder

- There are three inputs and eight outputs so we need 3-to-8-line decoder
- Two **OR** gates are required for logical **sum** of the desired minterms

 


Fig. 4-21 Implementation of a Full Adder with a Decoder


# Implementation of Full Adder with a Decoder

- A function with long list of minterms requires an OR gate with large number of inputs
- A function having a list of K minterms can be expressed in its **complemented** form  $F'$  with  $2^n - K$  minterms
- If the number of minterms in a function is greater than  $2^n/2$  then  $F'$  can be expressed with **fewer minterms**
- In such case it is advantageous to use a **NOR** gate to sum the minterms of  $F'$ . The output of the NOR gate **complements** this sum and generates the **normal** output F

# Problem Solving Session
 
### **Problem: 4-9**

A BCD-to-seven-segment decoder is a combinational circuit that converts a decimal digit in BCD to an appropriate code for the selection of segments in a display indicator used for displaying the decimal digit in a familiar form. The seven outputs of the decoder (a, b, c, d, e, f, g) select the corresponding segments in the display as shown in Fig. P4-9(a). The numeric display chosen to represent the decimal digit is shown Fig. P4-9(b). Implement your design with a 4:16 line Decoder constructed from two 3:8 line Decoders with enable input, one NOT gate and minimum number of external gates. The six invalid combinations should result in a blank display.



(a) Segment designation



(b) Numerical designation for display

**FIGURE P4-9**



### Solution:

Design procedure:

1. Derive the truth table that defines the required relationship between inputs and outputs.

w	x	y	z	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	X	0	0	0	0	0	0	0
1	1	X	X	0	0	0	0	0	0	0

2. Express the Boolean expressions for the outputs (a-g) in sum of minterms

$$a(w,x,y,z) = \Sigma(0,2,3,5,6,7,8,9)$$

$$b(w,x,y,z) = \Sigma(0,1,2,3,4,7,8,9)$$

$$c(w,x,y,z) = \Sigma(0,1,3,4,5,6,7,8,9)$$

$$d(w,x,y,z) = \Sigma(0,2,3,5,6,8,9)$$


$$e(w,x,y,z) = \Sigma(0,2,6,8)$$

$$f(w,x,y,z) = \Sigma(0,4,5,6,8,9)$$

$$g(w,x,y,z) = \Sigma(2,3,4,5,6,8,9)$$

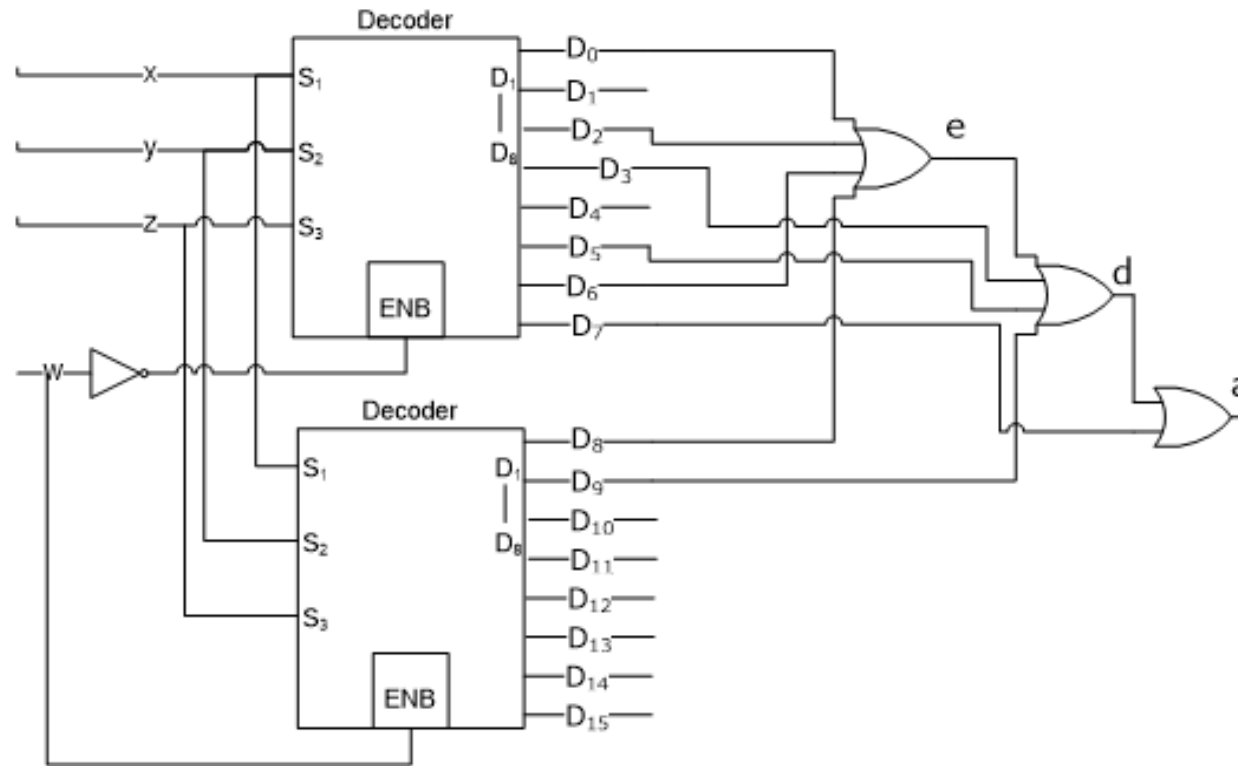3. Draw the logic circuit. Two 3-to-8-line decoders with enable inputs have been connected to form a 4-to-16-line decoder. Together they generate all the minterms of the input variables. OR gates are to be used to implement each of the functions a-g. The inputs to each OR gate are selected from the decoder outputs according to the list of minterm of each function.

The diagram below shows the circuit for output a, d and e. The same procedure should be followed to include the remaining functions and complete the logic circuit.



**Problem: 4-23**

Draw the logic diagram of a 2-to-4 line decoder using NOR gates only. Include an enable input.

**Solution:**

Design procedure:

1. The truth table for the circuit.

E	A	B	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1


$$D_0 = EA'B' = (E' + A + B)'$$

$$D_2 = EAB' = (E' + A' + B)'$$

$$D_1 = EA'B = (E' + A + B')'$$


$$D_3 = \underline{EAB} = (E' + A' + B')'$$

## 2. The logic diagram

 

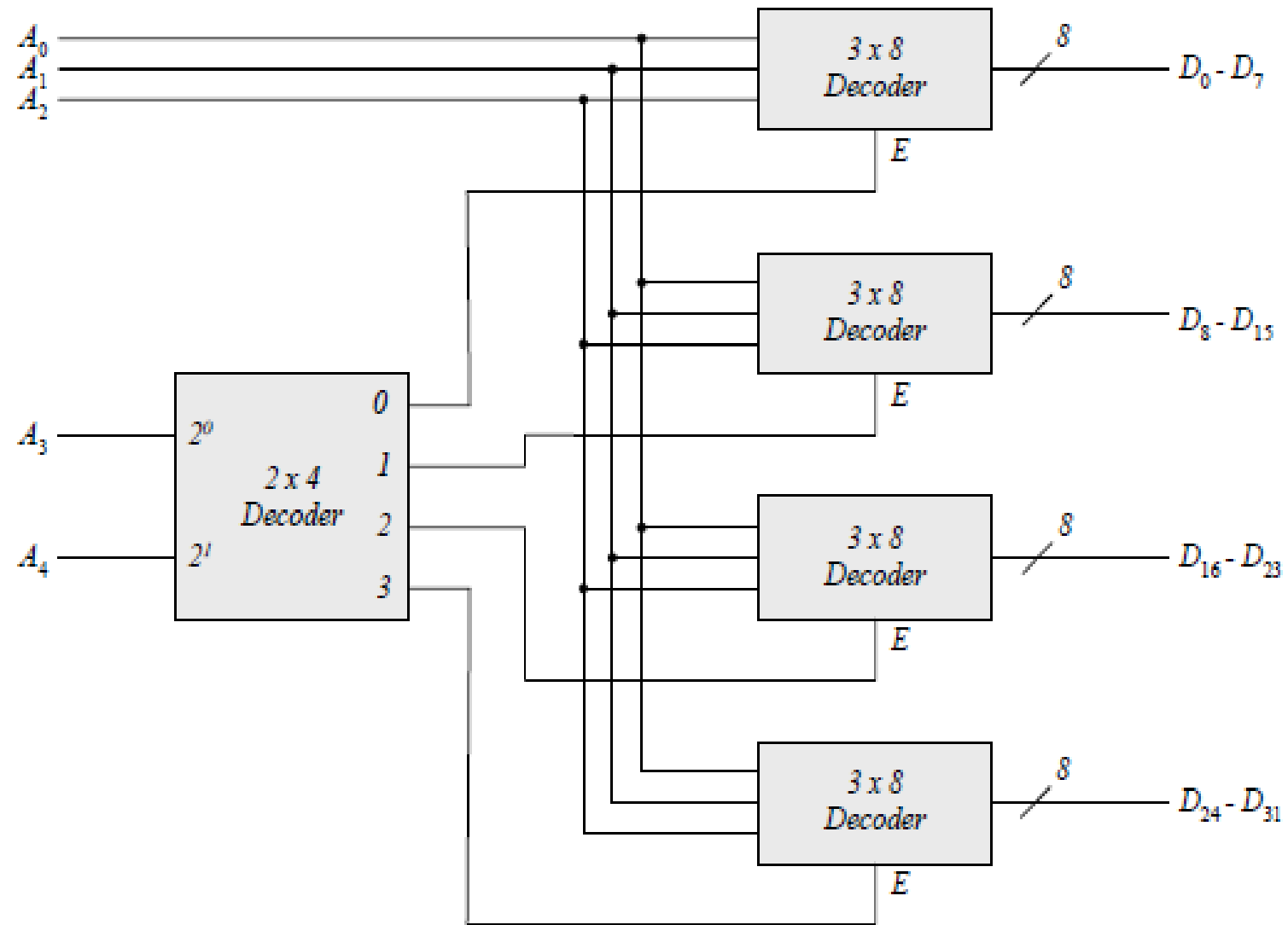Problem: 4-25

Construct a 5-to-32 line Decoder with four 3-to-8 line Decoders with an enable input and a 2-to-4 line Decoder. Use block diagrams for the components.



Problem: 4-27


CA combinational circuit is specified by the following three Boolean equations:-

$$F_1(A,B,C) = \Sigma(3,5,6)$$

$$F_2(A,B,C) = \Sigma(1,4,6)$$

$$F_3(A,B,C) = \Sigma(2,3,5,6,7)$$

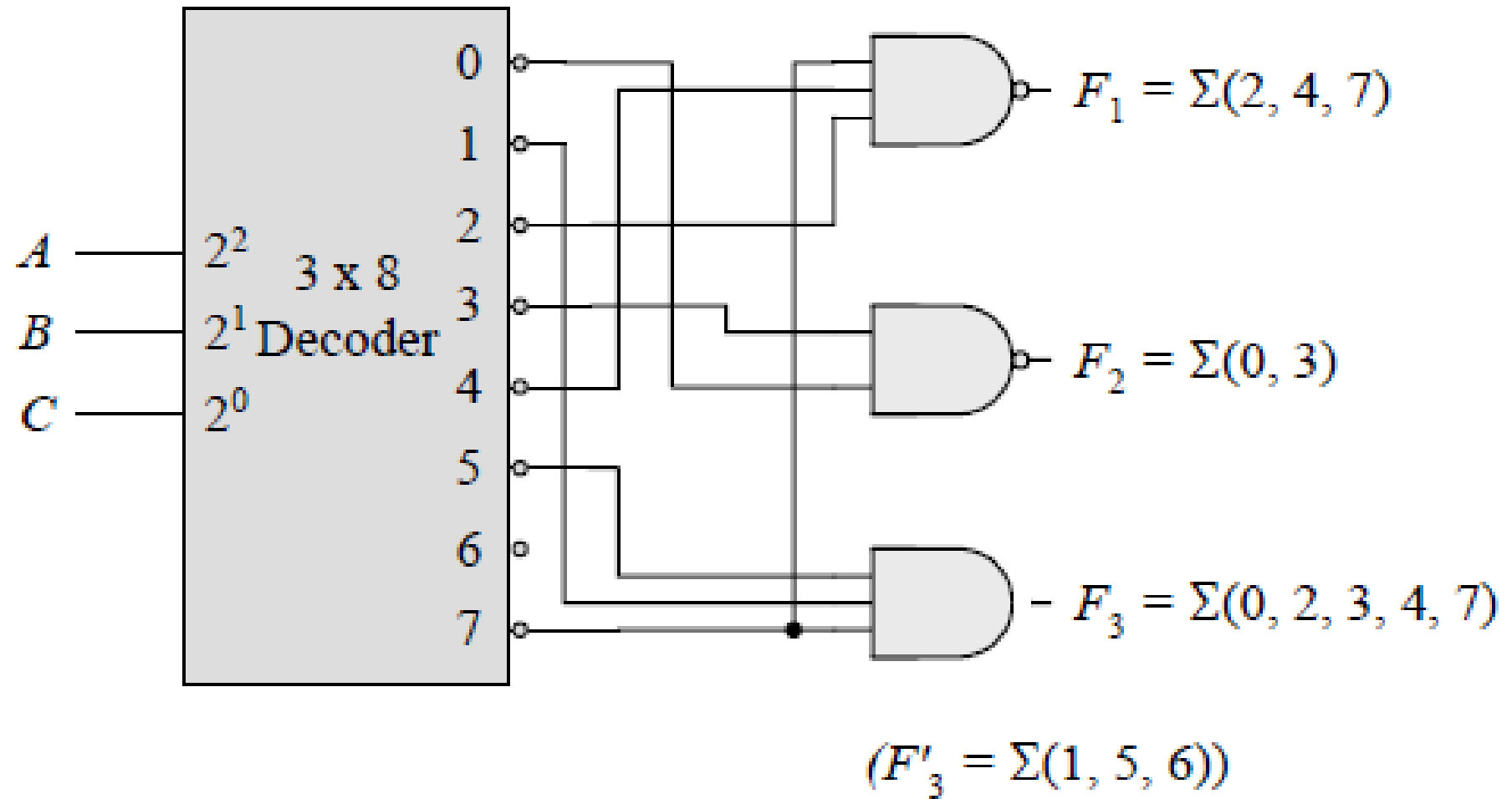Implement the circuit with a Decoder constructed with NAND gates and external NAND or AND gates connected to the Decoder outputs. Use a block diagram for the Decoder. Minimize the number of inputs in the external gates.





# The End