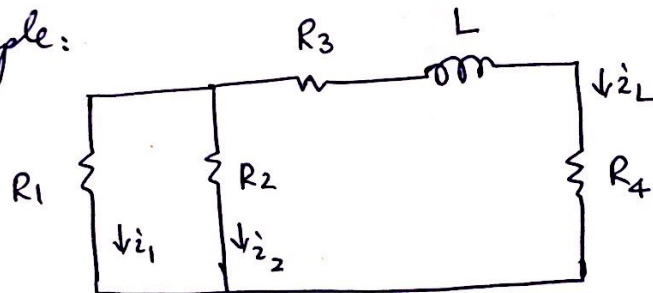


8.4 General RL/RC circuits (PP 275 8th Ed HKD)


The results obtained for the series RL/RC circuits can be extended to any number of resistors and inductors/capacitors if these can be reduced to one equivalent inductor/capacitor and a resistor.

— It is even possible to consider dependent sources.

— For example:



— Now R_{eq} faced by inductor is:

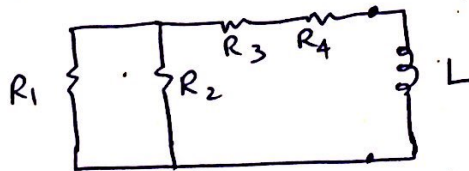

$$R_{eq} = R_3 + R_4 + (R_1 // R_2)$$


— Time constant is:-

$$\tau = \frac{L}{R_{eq}} \quad \text{or} \quad \frac{L}{R_{Th}}$$




— Also $\tau = \frac{L_{eq}}{R_{eq}}$

Example 8.4 General RL Circuit

(PP 277 8th Ed HKD)

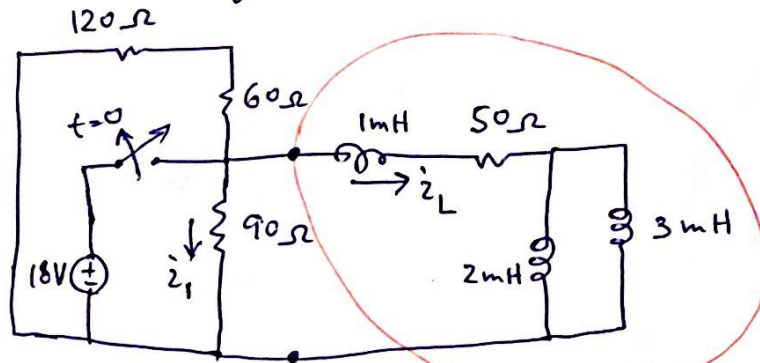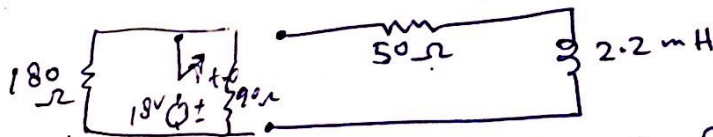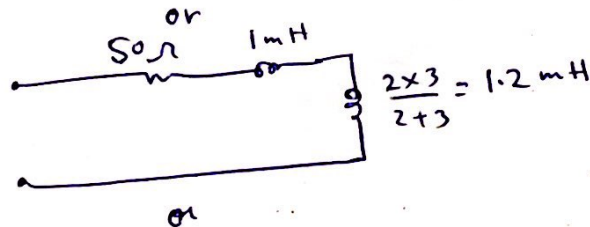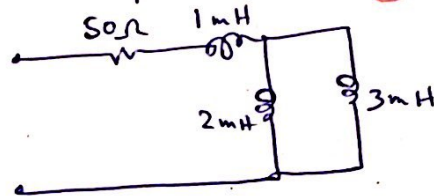
Determine i_1 and i_L for $t > 0$.Solution:

Can be simplified to:

So at $t=0$ switch is opened and R_{eq} seen by 2.2mH is:

$$R_{eq} = \frac{18 \times 90}{270} + 50$$

$$= 110 \Omega$$

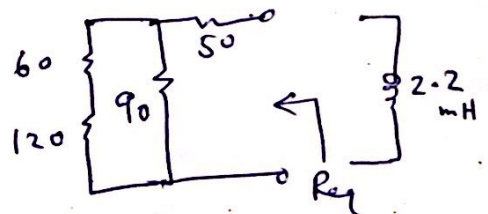

$$\text{Hence } \tau = \frac{L_{eq}}{R_{eq}} = \frac{2.2}{110} = 20\text{ms}$$

_____ contd


— contd (278)

therefore $\dot{i}_L(t) = A e^{-t/\tau} = A e^{-50,000t}$ amp (form of the natural response)

To determine coefficient 'A', at $t=0^-$

$$\dot{i}_L(0^-) = \frac{18}{50} = 360 \text{ mA} = \dot{i}_L(0^+)$$
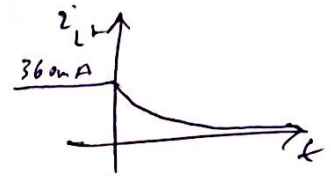
$$\text{So } \dot{i}_L = \begin{cases} 360 \text{ mA} & t < 0 \\ 360 e^{-50,000t} & t \geq 0 \end{cases}$$




Now for \dot{i}_1 for $t < 0$

$$\dot{i}_1 = \frac{18}{90} = 200 \text{ mA}$$

$$\text{Hence } \dot{i}_1 = \begin{cases} 200 \text{ mA} & t < 0 \\ ? & t \geq 0 \end{cases}$$

For $\dot{i}_1(0^+)$;

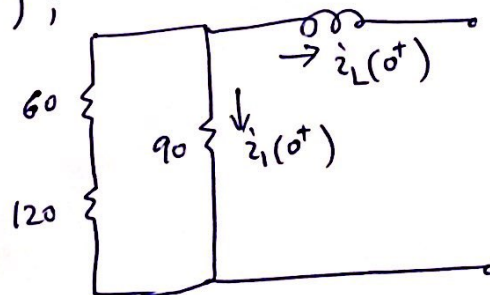

By CDR $\dot{i}_1(0^+) = -\dot{i}_L(0^+) \left(\frac{180}{180+90} \right)$


$$\dot{i}_1(0^+) = -240 \text{ mA}$$

— contd

— contd (27B)

$$\text{So } \dot{z}_1 = \begin{cases} 200 \text{ mA} & t < 0 \\ -240 e^{-50,000t} \text{ mA} & t \geq 0 \end{cases}$$

Graphically:

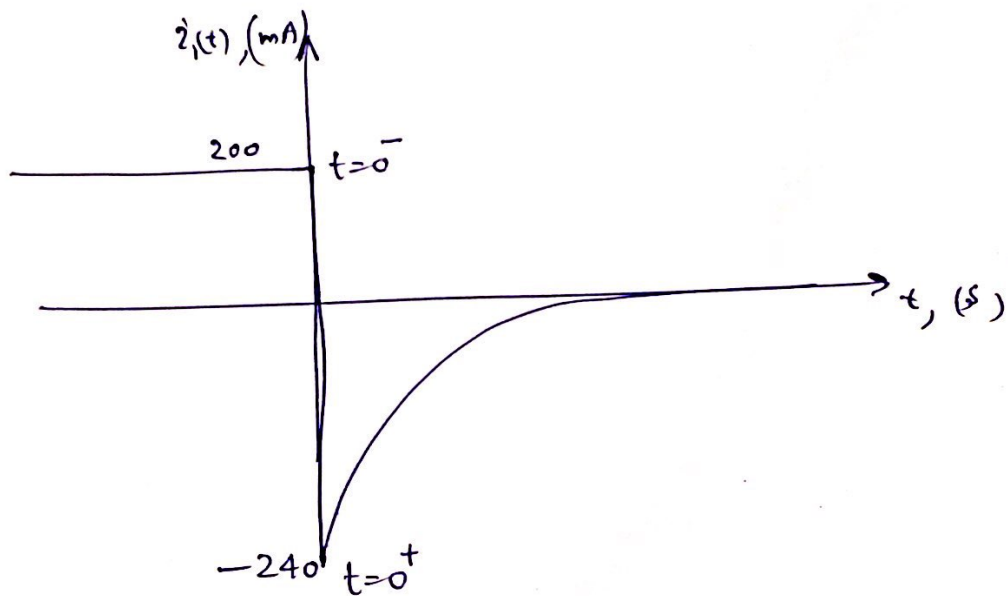

Imp:

Also :-
CDR

$$\dot{z}_1(t) = -\left(\frac{180}{180+90}\right)(360 e^{-50,000t}) \quad t \geq 0$$

$$\dot{z}_1(t) = -240 e^{-50,000t} \text{ mA}, \quad t \geq 0$$