

# EE-421: Digital System Design


## Doing MATHS on an FPGA

Arithmetic Circuit:  
(Revisiting) Adder – Carry Select Adder

Dr. Rehan Ahmed [rehan.ahmed@seecs.edu.pk]

# Aside: Combined Adder/Subtractor

$$A - B = A + B' + 1$$

 

Subtraction: Mode = 1

- B inputs are inverted
- Carry-in is 1

Addition: Mode = 0


- B inputs are NOT inverted
- Carry-in is 0

**Exercise: How does this affect delay?**

# Recall: 4-bit Ripple Carry Addition

A=0011

B=0101

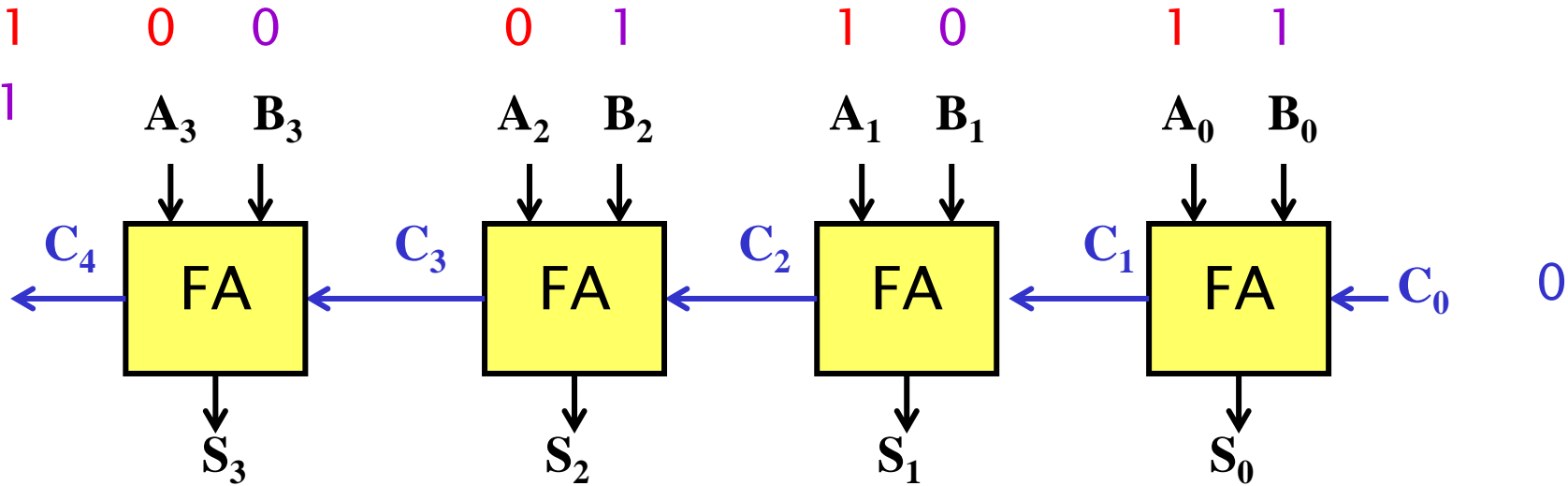

T=0	0	0	0	0	0	0	0	0	S=0000
T=1	0	0	0	1	0	1	1	0	S=0110
T=2	0	0	0	1	1	0	1	0	S=0100
T=3	0	0	1	0	1	0	1	0	S=0000
T=4	0	1	1	0	1	0	1	0	S=1000

$$\text{Delay} = 2(N-1)t_{PD} + 3t_{PD}$$

# 8-bit Ripple Carry Addition


- What's the delay for 8-bit ripple carry addition?

**Can we make Fast Adders i.e.  
Do something about the Carry Generation?**

# Carry Select Adder (CSA)

# Carry-Select Adder


- Basic Idea:
  - Trick for critical paths dependent on late input X
    - Precompute two possible outputs for  $X = 0, 1$
    - Select proper output when X arrives
- Carry-select adder **precomputes** n-bit sums
  - For **both possible** carries into **n-bit group**

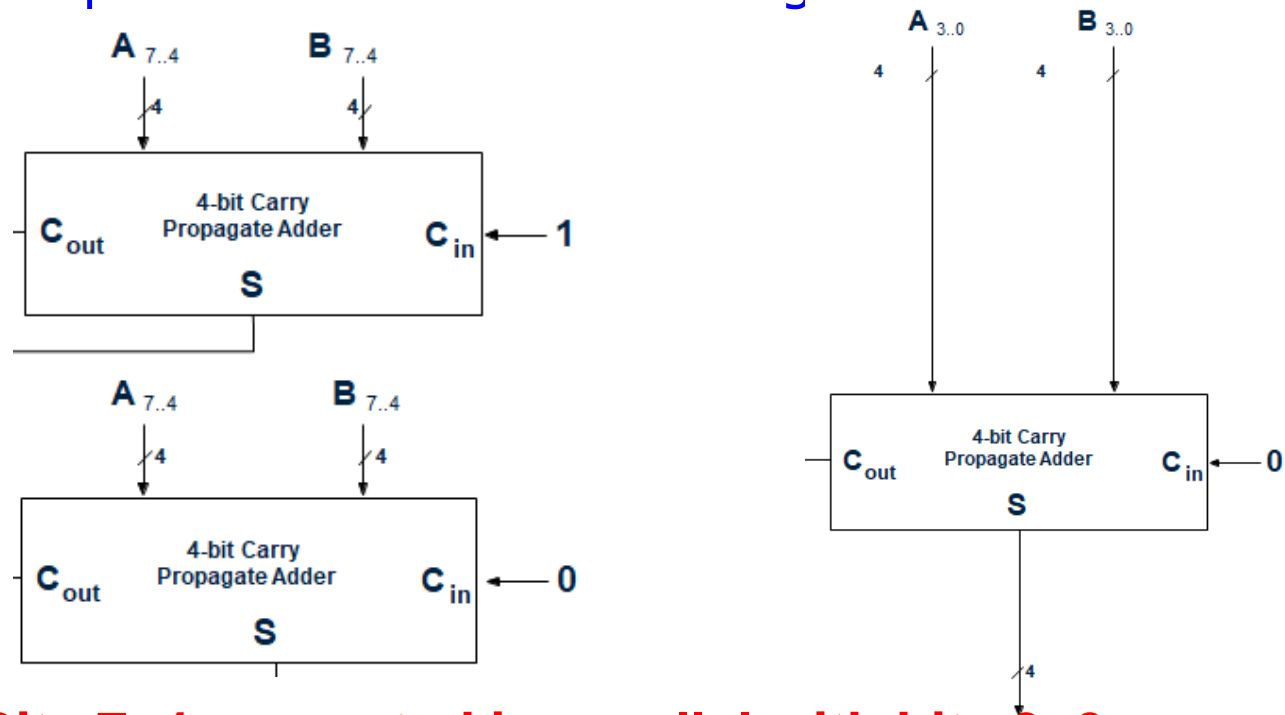

**Bits 7..4 computed in parallel with bits 3..0**
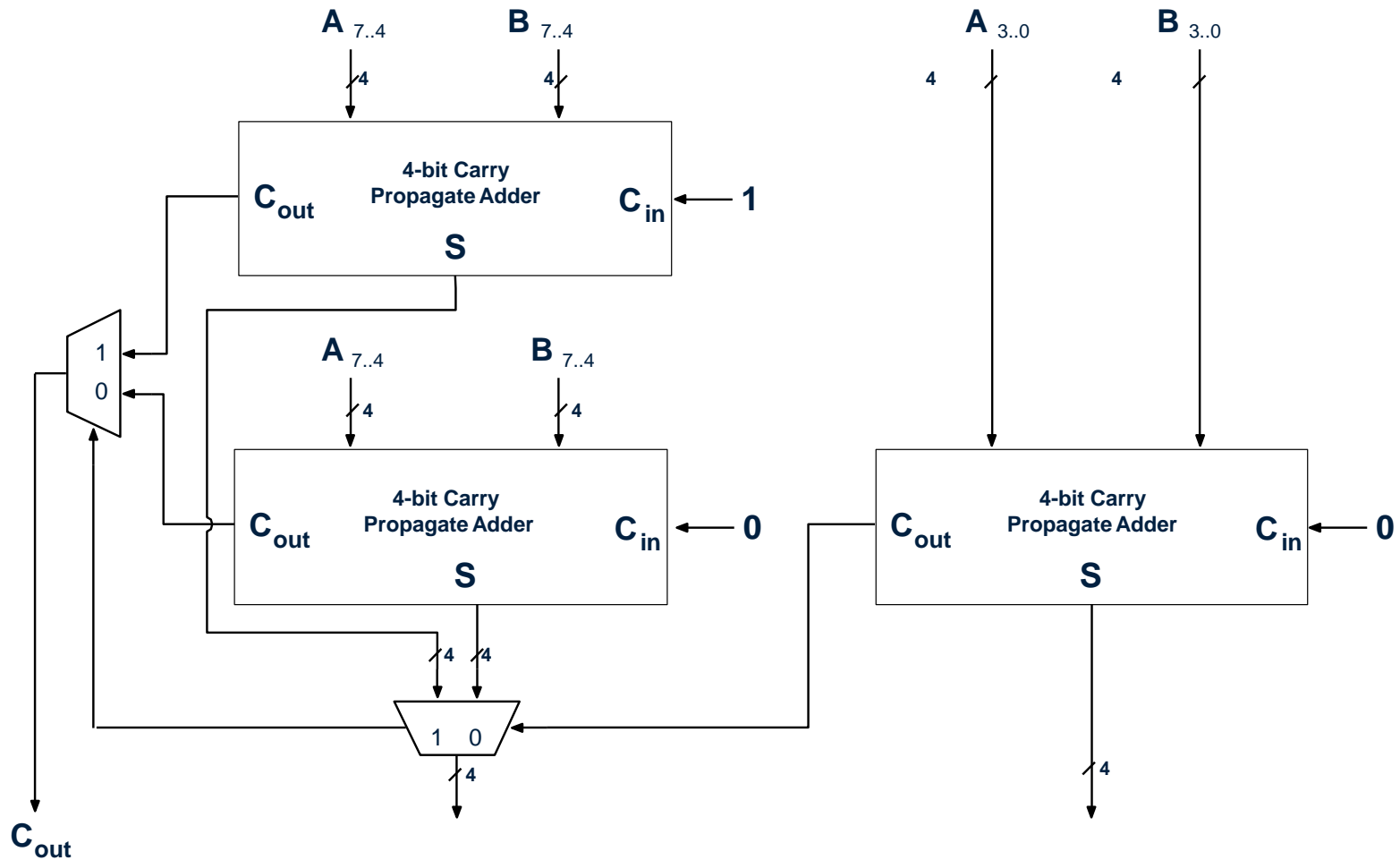
# Carry-Select Adder

- Then **select** the **correct** case when **carry-in** is **ready**
  - Trade-off area (use more gates) for faster performance




What's the delay for 8-bit addition using CSA?


 
# Recommended Reading

- Digital System Design with Verilog HDL, 3/e, b **S**tephen Brown and **Z**vonko Vranesic. [**S&Z**]
  - S&Z,
    - Chapter-3
      - 3.2



# THANK YOU

