
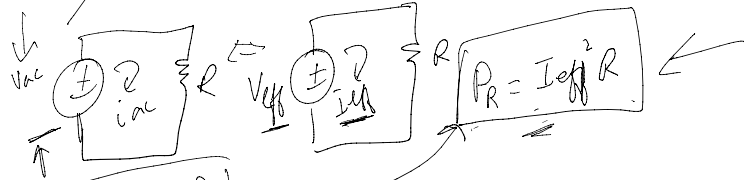


Effective value of any <sup>current</sup> waveform is a constant (DC-like value), which if passed through a Resistor 'R', delivers the same Average power as by the current waveform:

⇒ Voltage

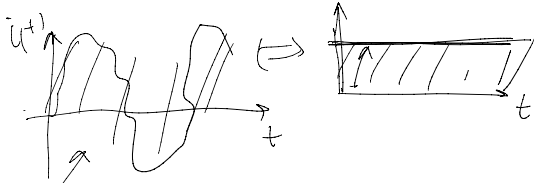

$$P_R = I_{eff}^2 R$$

$$\frac{1}{2} I_m^2 R = P_R$$

$$\frac{1}{2} I_m^2 R = I_{eff}^2 R$$

$$I_{eff} = \frac{I_m}{\sqrt{2}} = 0.707 \times I_m$$

$$\frac{1}{T} \int_0^T i_m^2(t) R dt = P_R$$


$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i_m^2(t) dt}$$

↓ RMS  
Root Mean Square

$$V_{rms} = \frac{V_m \times 0.707}{\sqrt{2}}$$

$$P = I_{rms}^2 R$$



$$= \frac{V_{rms}^2}{R}$$

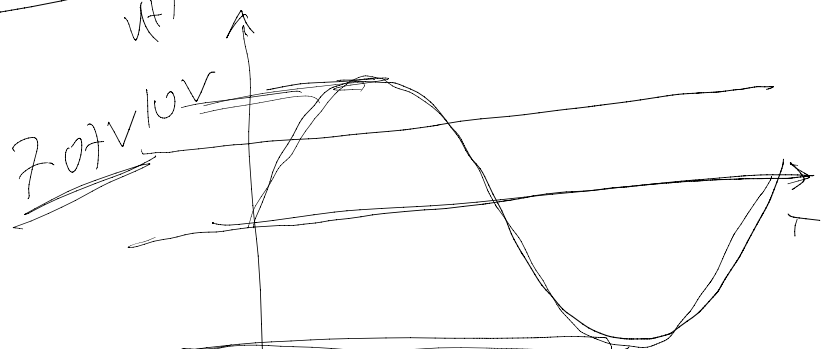

$$= \frac{V_{rms}^2}{R}$$

$$= I_{rms} \times V_{rms}$$

AC value

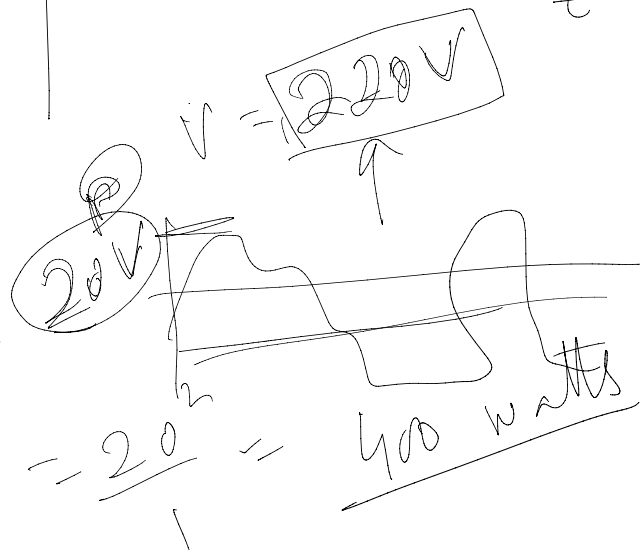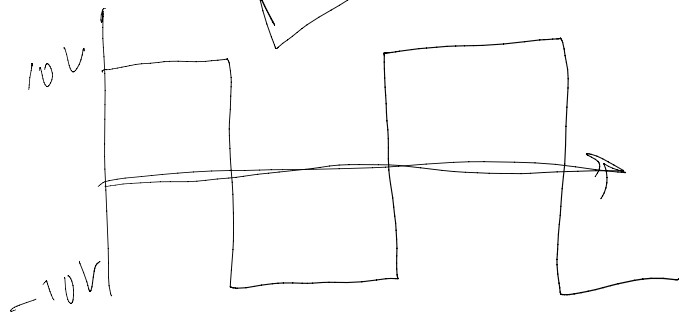

12