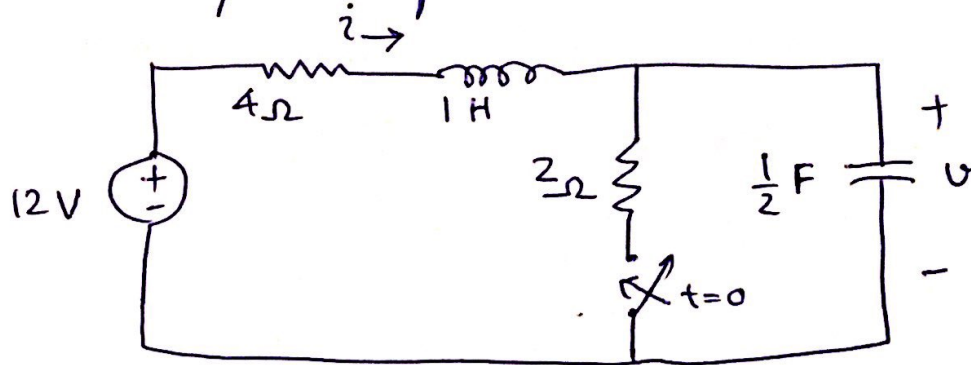



Example 8.9

Find the complete response ' v ' and then ' i ' for $t > 0$.



Solution: Let us first find the initial and the final values.


— When the switch is open and at $t < 0$

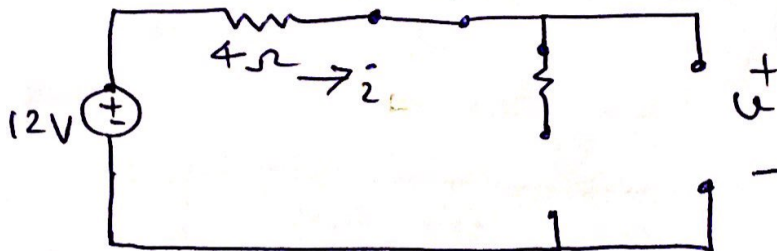

$$i(0^-) = 0$$

$$v(0^-) = 12V$$

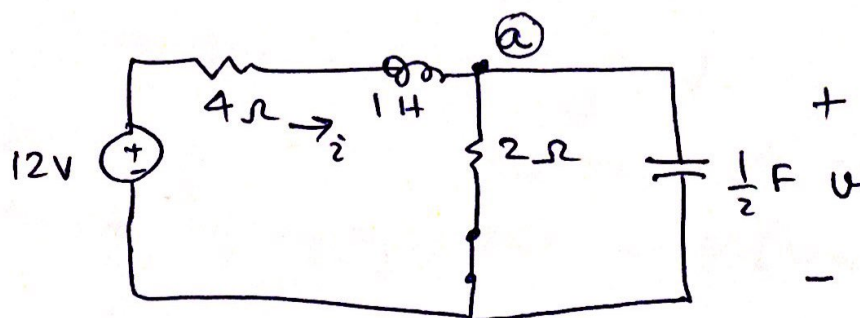— When the switch is closed and at $t > 0$



— Due to continuity $i(0^+) = i(0^-) = 0$

$$\text{and } v(0^+) = v(0^-) = 12V$$

_____ contd

(reiter)

— contd (340)

For more initial conditions, we apply KCL at node labelled (a).

$$\dot{i}(0^+) = \frac{v(0^+)}{2} + \dot{i}_c(0^+)$$

Putting $\dot{i}(0^+) = 0$

$v(0^+) = 12$ we get


$$0 = \frac{12}{2} + \dot{i}_c(0^+)$$

$$\dot{i}_c(0^+) = -6 \text{ A}$$

Now $\dot{i}_c(0^+) = C \frac{dv(0^+)}{dt}$

$$\text{or } \frac{dv(0^+)}{dt} = \frac{1}{C} \dot{i}_c(0^+) = \frac{1}{\frac{1}{2}} (-6) = -12 \text{ V/s}$$

— The final values are obtained

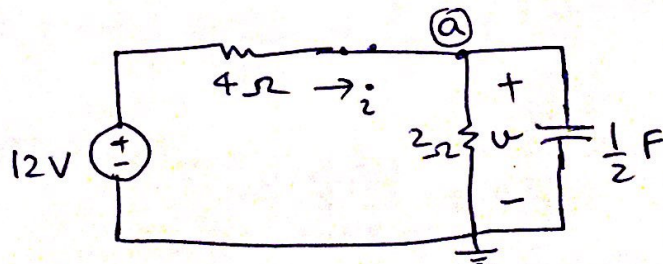

Now $i(\infty) = \frac{12}{4+2} = 2 \text{ A}$

So $v(\infty) = 2 \times 2 = 4 \text{ V}$.

— Next for $t > 0$, the transient response form is obtained by applying KCL at (a) (turning off 12V source)


$$\dot{i} = \frac{v}{2} + C \frac{dv}{dt} = \frac{v}{2} + \frac{1}{2} \frac{dv}{dt}$$

— contd

(Optional)
(neither)

— could (340)

Applying KVL to the left mesh,

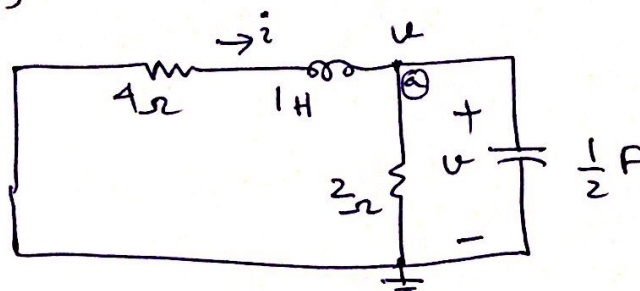

(obtaining the form for
transient response)

$$4i + 1 \times \frac{di}{dt} + u = 0$$

— because we are interested in u , we substitute i .

$$\text{Now } i = \frac{u}{2} + \frac{1}{2} \frac{du}{dt}$$

$$\text{So } 4 \frac{u}{2} + \frac{4}{2} \frac{du}{dt} + \frac{1}{2} \left(\frac{du}{dt} + \frac{d^2 u}{dt^2} \right) + u = 0 \quad \times 2$$

$$4u + 4 \frac{du}{dt} + \frac{du}{dt} + \frac{d^2 u}{dt^2} + 2u = 0$$

Arranging

$$\frac{d^2 u}{dt^2} + 5 \frac{du}{dt} + 6u = 0$$

— The characteristic equation is

$$s^2 + 5s + 6 = 0$$

— The roots are $s = -2$ and $s = -3$.

— Thus the natural response is

$$u_n(t) = A e^{-2t} + B e^{-3t}$$

— could

(Optional)
(neither)

— cold (340)

$$\text{Now } U_{ss}(t) = U(\infty) = 4$$

So the complete response is:-

$$U(t) = U_{ss}(t) + U_t$$
$$U(t) = 4 + A e^{-2t} + B e^{-3t}$$

— Using initial conditions

$$U(0) = 12$$

$$\text{So } 12 = 4 + A + B$$

$$A + B = 8$$

①

— And

$$\frac{dU}{dt} = -2A e^{-2t} - 3B e^{-3t}$$

$$\frac{dU}{dt} \text{ at } t=0 \text{ is } -12 \text{ V/s}$$

$$\text{So } -12 = -2A - 3B$$

$$2A + 3B = 12$$

②

— Solving ① and ②

$$A = 12$$

$$B = -4$$

Hence

$$U(t) = 4 + 12e^{-2t} - 4e^{-3t} \text{ V, } t > 0$$

— Now to obtain i , we know

$$i = \frac{U}{Z} + \frac{1}{Z} \frac{dU}{dt}$$

— cold

(Optional)
(neither)

— contd (341)

$$\text{So } \dot{z} = \frac{4 + 12e^{-2t} - 4e^{-3t}}{2} + \frac{1}{2}(-24e^{-2t} + 12e^{-3t})$$

$$\dot{z} = 2 + 6e^{-2t} - 2e^{-3t} - 12e^{-2t} + 6e^{-3t}$$

$$\dot{z} = 2 - 6e^{-2t} + 4e^{-3t} \quad A, \quad t > 0$$

Note $\dot{z}(0) = 0$

_____ 