



NATIONAL UNIVERSITY OF SCIENCES & TECHNOLOGY

Electronic Devices & Circuits (EE-215)

Assignment # 2

Diodes

Submitted to: Dr. Shakeel Alvi

Submitted by: Muhammad Umer

Class: BEE-12C

Semester: 4th

Dated: 20/03/2022

CMS ID: 345834


• Assignment 2

EE - 215

Muhammad Umer - 345834


D 4.15

Figure
E 4.15

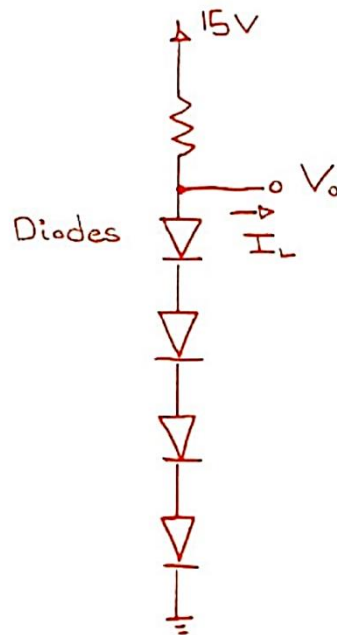

a)

Small Signal Model

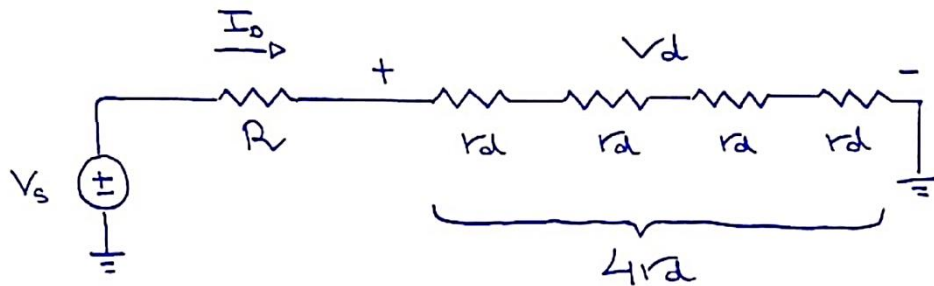

Given that $\Delta V_d = 20 \text{ mV}$ for $\Delta I_d = 1 \text{ mA}$;

And without any load , i.e. $I_L = 0$, $V_{out} = V_d$

\therefore Using $r_d = \frac{\partial V_d}{\partial I_d}$

$$\Rightarrow 4r_d = \frac{20 \text{ mV}}{1 \text{ mA}} = 20 \Omega$$

$$\Rightarrow \boxed{r_d} = \frac{20}{4} \Omega = \underline{5 \Omega}$$

- The diode current I_0 can then be calculated as:

$$\bullet \quad r_d = \frac{V_T}{I_0} \Rightarrow I_0 = \frac{V_T}{r_d}$$

$$\Rightarrow \boxed{I_0} = \frac{25 \text{ mV}}{5 \Omega} = \underline{5 \text{ mA}}$$

- The current through R is the same as I_0 .

$$\Rightarrow \frac{15 - V_{\text{out}}}{R} = I_0 \Rightarrow \frac{15 - 3}{R} = 5 \text{ mA}$$

$$\Rightarrow \boxed{R} = 2400 \Omega = \underline{2.4 \text{ k}\Omega} \quad \left| \begin{array}{l} \text{Part} \\ (a) \end{array} \right.$$

b)

Saturation Current

- We know that;

$$I_0 = I_s e^{V_D/V_T}$$

\therefore (where V_D is the voltage across a single diode)

$$V_{D(\text{single})} = \frac{V_d}{4} = \frac{3}{4}$$

$$\Rightarrow I_s = I_0 e^{-V_0/V_T}$$

$$I_s = (5 \text{ mA}) e^{-(3/4)/25 \text{ mV}}$$

$$\boxed{I_s} = \underline{41.678 \times 10^{-16} \text{ A}} \quad \left| \begin{array}{l} \text{Part} \\ (b) \end{array} \right.$$

c)

Change in Voltage

For exponential models:

$$V_2 - V_1 = 2.3 V_T \log_{10} (I_2/I_1)$$

$$\text{or } \Delta V_0 = 2.3 V_T \log_{10} (I_2/I_1) \quad (*)$$

- If the load draws $I_L = 1 \text{ mA}$ from the regulator, we observe a decrease of 1 mA from I_0 without load.
- $\underline{I_2 = I_0 - 1 \text{ mA} = 5 \text{ mA} - 1 \text{ mA} = 4 \text{ mA}}$
Substituting $I_2 = 4 \text{ mA}$ and $I_1 = I_0 = 5 \text{ mA}$ in (*)

$$\Rightarrow \Delta V_0 = 2.3 (25 \text{ mV}) \log_{10} \left(\frac{4 \text{ mA}}{5 \text{ mA}} \right)$$

$$\underline{\Delta V_D = -5.572 \times 10^{-3} \text{ V}}$$

- Which is the change in voltage across a single diode

- As we have L_1 diodes in series, the total change in output voltage is ;

$$\Delta V_o = L_1 \Delta V_D = -22.28 \times 10^{-3} V$$

$$\boxed{\Delta V_o} = -22.28 \text{ mV} \quad \left| \begin{array}{l} \text{Part} \\ (c) \end{array} \right.$$

20/03
2022

ENED

Chun
