

9.4 The Underdamped Parallel RLC Circuit: $\alpha < \omega_0$ (PP 338 8th Ed HKD)

When we continue to increase R , we get an underdamped response.

— The damping coefficient $\alpha = \frac{1}{2RC}$ decreases while ω_0 remains constant.

— Thus α^2 becomes smaller than ω_0^2 and the radicand ($\sqrt{\alpha^2 - \omega_0^2}$) becomes negative.

— Let us start with general response:—

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\text{where } s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\begin{aligned} \text{Now } \sqrt{\alpha^2 - \omega_0^2} &= \sqrt{-1} \sqrt{\omega_0^2 - \alpha^2} \\ &= j \sqrt{\omega_0^2 - \alpha^2} \end{aligned}$$

$$\text{where } j \equiv \sqrt{-1}$$

— the new radical, real for the underdamped case is called ω_d , the natural resonant frequency:

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$\text{So } s_{1,2} = -\alpha \pm j\omega_d$$

also

ω_0 = undamped natural frequency

ω_d = damped natural frequency

— The response may be written as:

$$v(t) = e^{-\alpha t} (A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t})$$

————— Contd

— contd (339)

— It can also be written as:-

$$u(t) = e^{-\alpha t} \left\{ (A_1 + A_2) \left[\frac{e^{j\omega t} + e^{-j\omega t}}{2} \right] + j(A_1 - A_2) \left[\frac{e^{j\omega t} - e^{-j\omega t}}{j2} \right] \right\}$$

$$\text{so } u(t) = e^{-\alpha t} \left[(A_1 + A_2) \cos \omega t + j(A_1 - A_2) \sin \omega t \right]$$

— The multiplying factors may be assigned new symbols :-

$$u(t) = e^{-\alpha t} \left[B_1 \cos \omega t + B_2 \sin \omega t \right]$$

— The two real constants B_1 and B_2 are selected to fit the given initial conditions.

(Note: Euler's identity $e^{j\theta} = \cos \theta + j \sin \theta$)

$$\text{and } e^{-j\theta} = \cos \theta - j \sin \theta$$

— B_2 is real. Don't be misled by

$$B_2 = j(A_1 - A_2) \Rightarrow$$

A_1 and A_2 are complex conjugates.


(PP 316 Nilsson & Riedel)

— Also $\cos \omega t = \frac{e^{j\omega t} + e^{-j\omega t}}{2}$

$$\text{and } \sin \omega t = \frac{e^{j\omega t} - e^{-j\omega t}}{j2}$$

Example: The Underdamped Parallel RLC circuit
(PP 339 8th Ed HKD)

Determine $v(t)$.

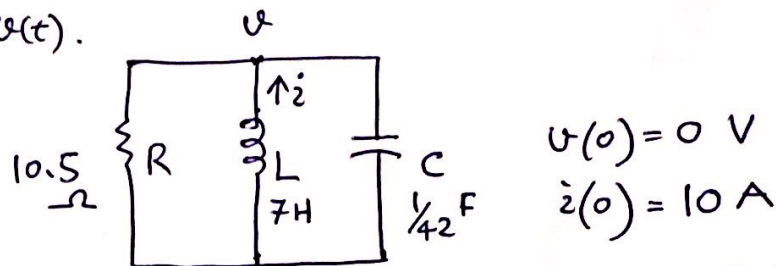

Note: R has been increased from 6Ω to 8.57Ω to 10.5Ω .

Solution: As it is identified as a parallel RLC circuit,
so $\alpha = \frac{1}{2RC} = 2 s^{-1}$ ($\alpha = \frac{R}{2L}$ for series RLC)

and $\omega_0 = \frac{1}{\sqrt{LC}} = \sqrt{6} s^{-1} = 2.45 s^{-1}$

because $\alpha < \omega_0$

So we determine

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{2} \text{ rad/s}$$

— The response will be of the form

$$v(t) = e^{-2t} (B_1 \cos \sqrt{2} t + B_2 \sin \sqrt{2} t)$$

— To determine initial B_1 and B_2 .

At $v(0) = 0$

so

$$0 = B_1 \quad (\text{because } \sin 0 = 0)$$

Hence

$$v(t) = e^{-2t} (B_2 \sin \sqrt{2} t) \quad \text{--- ①}$$

contd.

— contd (340)

Now derivative of $u(t)$ is

$$\frac{du}{dt} = \sqrt{2} B_2 e^{-2t} \cos \sqrt{2} t - 2 B_2 e^{-2t} \sin \sqrt{2} t$$

At $t=0$

$$\left. \frac{du}{dt} \right|_{t=0} = \frac{\dot{u}_c(0)}{C} = 420 \quad (\text{calculated earlier})$$

$$\text{So } 420 = \sqrt{2} B_2 \quad (\sin 0 = 0 \text{ and } \cos 0 = 1)$$

$$\text{or } B_2 = \frac{420 \cdot \sqrt{2}}{\sqrt{2} \cdot \sqrt{2}} = 210\sqrt{2}$$

— Putting the value in ①

$$u(t) = e^{-2t} 210\sqrt{2} \sin \sqrt{2} t$$

$$\text{or } u(t) = 210\sqrt{2} e^{-2t} \sin \sqrt{2} t \quad \checkmark$$
