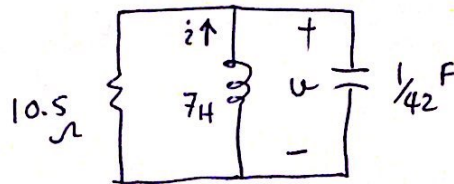


Graphical Representation of the Underdamped Response

(PP 340 8th Ed HKD)

For the parallel RLC ckt




$$v(0) = 0$$

$$i(0) = 10 \text{ A}$$

$$v(t) = 210\sqrt{2} e^{-2t} \sin \sqrt{2} t$$

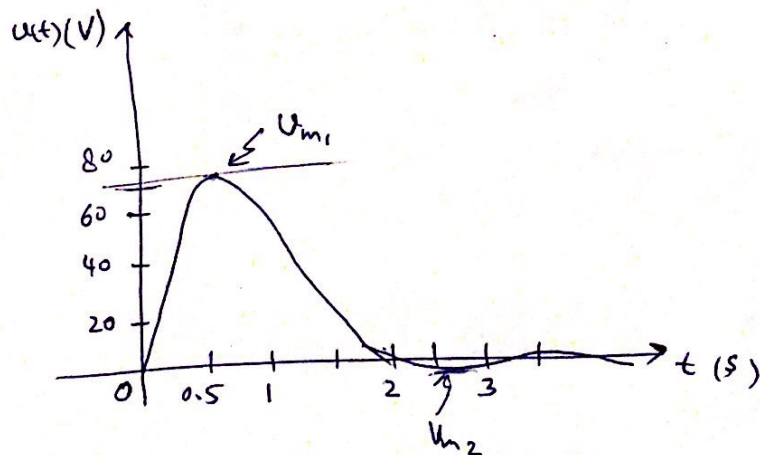- the response function has an initial value of zero, because of the initial condition i.e. $v(0) = 0$
- and a final value of zero because the exponential term vanishes for large values of t .
- The response curve can be drawn as:-




- In this example, the response is only slightly underdamped
- The oscillatory nature of the response becomes more noticeable as α decreases.

_____ contd

— contd (341)

If $\alpha = 0$, which corresponds to $R \rightarrow \infty$, then $u(t)$ is an undamped sinusoid that oscillates with constant amplitude.

— The different values of R will yield:-

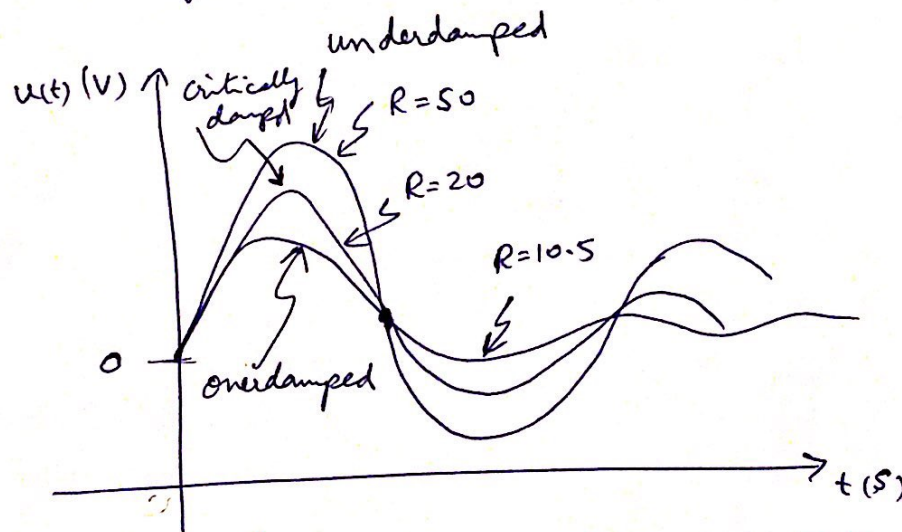

(Fig 9-15 Showing increase in oscillatory behaviors as R increases)

AK