# Lab 13: Programming 8051 Microcontroller

EE222: Microprocessor Systems

## 1 Administrivia

## **Learning Outcomes**

By the end of this lab you will be able to;

- 1. Write an assembly language code for x86 architecture
- 2. Create .hex file using Keil µVision IDE
- 3. Burn your code onto 8051 microcontroller to run your application successfully

### **Deliverable**

You are required to submit

- Appropriately Commented Code
- Explicit Calculations for Timer Values
- Issues in Developing the Solution and your Response

in the beginning of next lab

#### **Hardware Resources**

• This is a Proteus based simulation lab and does not require any hardware.

#### Introduction

The AT89C51 is an age old 8-bit microcontroller from the Atmel family. It works with the popular 8051 architecture and hence is used by most beginners till date. It is a 40 pin IC package with **4 Kb flash memory**. It has **four ports** and all together provides **32 Programmable GPIO pins**. It does not have in-built ADC module and supports only USART communication. Figure 1 shows the pin-out of 8051 microcontroller.

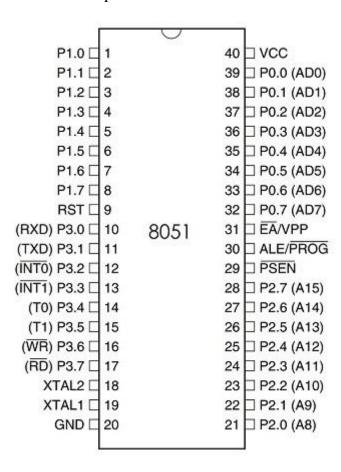


Figure 1. 8051 Microcontroller Pin-out

In order to program the Atmel microcontroller we will need

- **IDE** (Integrated Development Environment), where the programming takes place.
- Compiler, where our program gets converted into MCU readable form called HEX files.
- **IPE** (Integrated Programming Environment), which is used to dump our hex file into our MCUs.

We will be using **Keil uVision IDE** throughout this lab. Use the provided "*How to Program with Keil*" file to familiarize yourself with the Keil environment.

## LED Interfacing with 8051

For any microcontroller, LED interfacing is equivalent to "Hello world!" program to see a physical output. We will begin by learning how to interface an LED with 8051 microcontroller.

Figure 2 shows the circuit diagram of two LEDs interfaced with AT89C51 on two different Port Pins. One is connected to Pin7 of Port0 and second one is connected to Pin0 of Port2. Both LEDs are driven through resistors to limit the current.

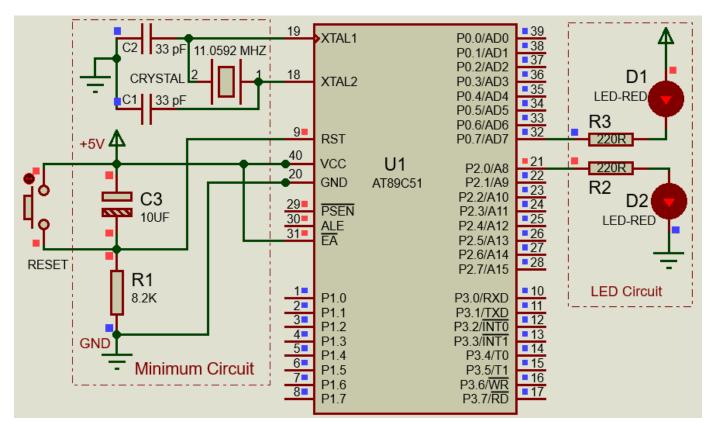


Figure 2. LED interfacing with 8051

Note that the "Minimum Circuit" on the left is required to provide external clock to the 8051 microcontroller.

#### Lab Task

Build the following <u>code</u> in Keil to generate a hex file. Understand its functionality. Then construct the circuit of figure 2 in Proteus and burn the created hex file. Observe the output.

```
ORG
               00H
                               ; PROGRAM STORE LOCATION
       MOV
               P0,#00H
                               ; REFRESHING PORT-0
       MOV
               P1,#00H
                               ; REFRESHING PORT-1
               P2,#00H
                               ; REFRESHING PORT-2
       MOV
       MOV
               P3,#00H
                               ; REFRESHING PORT-3
AGAIN:
       CLR
               P0.7
                               ; PORT-0 PIN-7 LOW (LED1-ON)
               P2.0
                               ; PORT-2 PIN-0 HIGH (LED2-ON)
       SETB
       LCALL
              DELAY
                               ; CALL DELAY SUBROUTINE
               P0.7
                               ; PORT-0 PIN-7 HIGH (LED1-OFF)
       SETB
                               ; PORT-2 PIN-0 LOW (LED2-OFF)
       CLR
               P2.0
        LCALL
               DELAY
                               ; CALL DELAY SUBROUTINE
                               ; LOOP FOREVER TO LABEL AGAIN
        LJMP
               AGAIN
DELAY:
                               ; DELAY SUBROUTINE
       MOV
               R7,#50
L3 :
       MOV
               R6,#100
L2 :
       MOV
               R5,#100
L1 :
               R5,L1
       DJNZ
       DJNZ
               R6,L2
        DJNZ
               R7,L3
        RET
                               ; END DELAY SUBROUTINE
        END
```

## **ADC Interfacing with 8051**

Refer to the following <u>link</u> to interface an AD0804 ADC chip with 8051 microcontroller to read analog signals. As a part of **lab task**, build the following circuit in Proteus and load the provided assembly <u>code</u> to faithfully run the analog-to-digital conversion.

